

Code No: 182AC

R22

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year II Semester Examinations, September - 2023

BASIC ELECTRICAL ENGINEERING

(Common to ECE, EIE, CSE (AI&ML), CSE(IOT), AI&DS, AI&ML)

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.

i) Part - A for 10 marks, ii) Part - B for 50 marks.

- Part-A is a compulsory question which consists of ten sub-questions from all units carrying equal marks.
- Part-B consists of ten questions (numbered from 2 to 11) carrying 10 marks each. From each unit, there are two questions and the student should answer one of them. Hence, the student should answer five questions from Part-B.

PART - A

(10 Marks)

- 1.a) Draw the equivalent circuit of Norton's theorem. [1]
- b) Write the time constant of RC circuit. [1]
- c) Define Peak factor. [1]
- d) Write the line voltage and phase voltage relation in star connections. [1]
- e) What is ideal transformer? [1]
- f) The efficiency of the transformer is high compared to other electrical machines. Give the reason. [1]
- g) What are the parts of synchronous generator? [1]
- h) Define Slip. [1]
- i) Differentiate ELCB and MCCB. [1]
- j) Differentiate fuse and earthing. [1]

PART - B

(50 Marks)

- 2.a) Find the power supplied by the 2V source in the circuit shown below. (Figure 1)

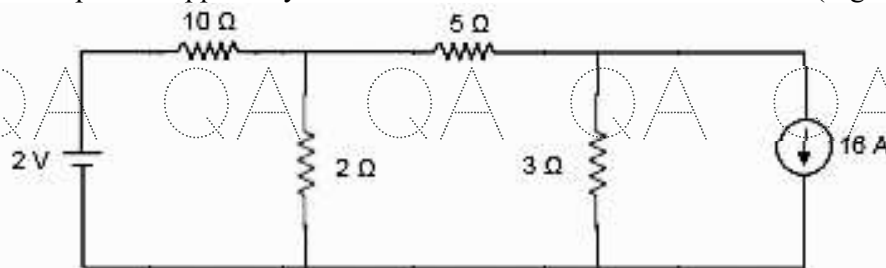


Figure 1

- b) A capacitor in an RC circuit with $R = 25 \text{ Ohm}$ and $C = 50 \text{ micro Fared}$ is being charged with initial zero voltage. What is the time taken for the capacitor voltage to reach 40 percentage of its steady state value? [5+5]

OR

