

R16

Code No: 131AK

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year I Semester Examinations, January/February - 2025

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to EEE, ECE, CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART – A

(25 Marks)

- 1.a) Define and draw about the Independent and Dependent Sources. [2]
- b) What is RMS value and Average Value? [3]
- c) Write the Statement for Superposition Theorem. [2]
- d) What is Resonance? Give any one example. [3]
- e) What is Diffusion Capacitance of diode? [2]
- f) Define Ripple Factor. [3]
- g) What is a Transistor? Draw its symbol. [2]
- h) In a common base connection, the emitter current is 2mA. If the emitter circuit is open, the collector current is $55 \mu\text{A}$, $\alpha = 0.92$. Find the total collector current. [3]
- i) What is Pinch-Off Voltage? [2]
- j) Write any two advantages of Junction Field Effect Transistor. [3]

PART – B

(50 Marks)

- 2.a) Briefly discuss about the Phase and Phase Difference, Power Factor, Complex and Polar Forms.
- b) Write short notes on Kirchoff's Laws and Source Transformation. [5+5]

OR

- 3.a) Using Nodal analysis determine node voltages for the below circuit. (Figure 1)

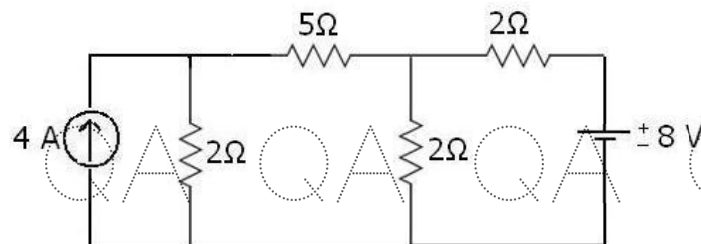


Figure 1

- b) Briefly discuss about the steady state analysis of a series RLC circuit with sinusoidal excitation. [5+5]

- 4.a) Derive and discuss about the Bandwidth and Quality Factor of a series resonant R-L-C circuit.
- b) A series RLC circuit is connected across a variable frequency supply and has $R = 12 \text{ ohms}$, $L = 1 \text{ mH}$ and $C = 1000 \text{ pF}$. Calculate (i) Resonant frequency, (ii) Q factor and (iii) Half power frequencies. [5+5]

OR

- 5.a) Find the current flowing through the $1\text{K}\Omega$ resistor of the network shown below figure 2 by using Norton's theorem.

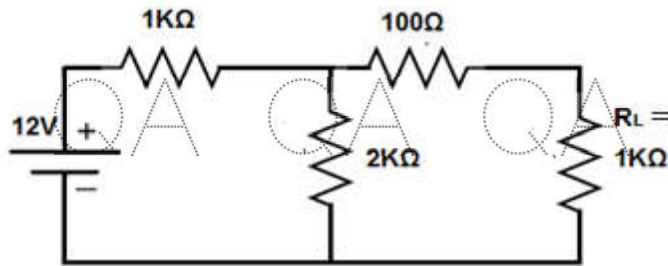


Figure 2

- b) Write the statement of Reciprocity Theorem and verify the following circuit (Figure 3). [5+5]

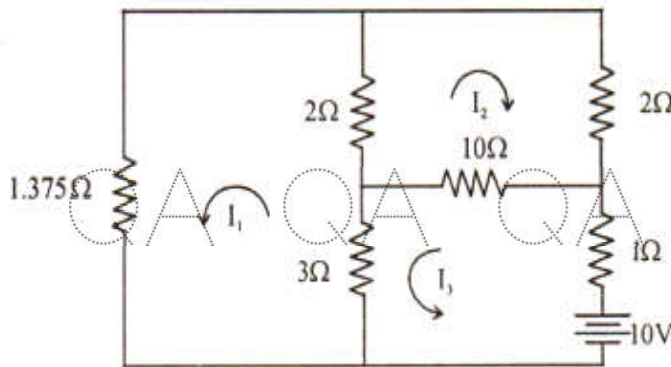


Figure 3

- 6.a) Discuss and draw the VI characteristics of Zener Diode.
- b) Briefly discuss about Transition Capacitance of a semiconductor diode. [5+5]

OR

- 7.a) Draw and discuss the Half Wave Rectifier with and without filter.
- b) Briefly discuss about π section filter with neat circuit diagram. [5+5]

8. Draw and discuss the operation of Common Emitter Configuration of Transistor and draw its output and input characteristics. [10]

OR

9. Discuss how to determine h-parameters of a Transistor. [10]

- 10.a) Explain the Volt-Ampere characteristics of JFET.
- b) Compare and discuss about BJT & FET. [5+5]

OR

11. Draw and discuss clearly about the construction and operation of N- Channel JFET and also describe about drain characteristics. [10]