

R18

Code No: 152AC

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year II Semester Examinations, February - 2025

BASIC ELECTRICAL ENGINEERING

(Common to ECE, EIE, CSBS, CSE(AI&ML), CSE(IOT), AI&DS, AI&ML)

Time: 3 Hours

Max. Marks: 75

- Note:** i) Question paper consists of Part A, Part B.
ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.
iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART - A

(25 Marks)

- | | | |
|------|---|-----|
| 1.a) | Define a current source. | [2] |
| b) | Define ohm's law. How voltage and current are related in resistor? | [3] |
| c) | What is the use of reactive power? | [2] |
| d) | How line quantities are related to phase quantities in a 3-phase star connection? | [3] |
| e) | Draw star-delta transformer connection. | [2] |
| f) | How to reduce core losses? | [3] |
| g) | What is meant by separate excitation in d.c machines? | [2] |
| h) | What are the applications of 3-phase Induction Motor? | [3] |
| i) | What is meant by switchgear? | [2] |
| j) | State different wires. What are the applications of wires? | [3] |

PART - B

(50 Marks)

2. In the circuit below (figure 1), find the currents, voltages and powers in all the circuit elements. [10]

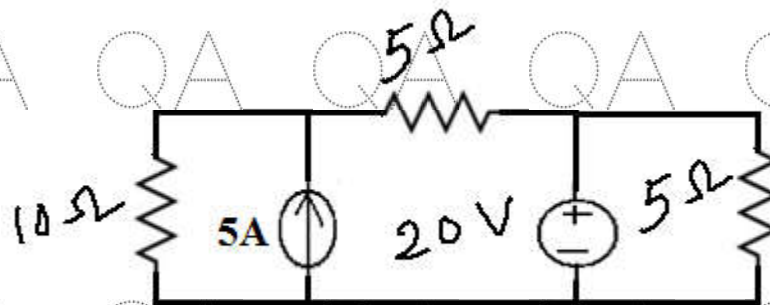


Figure 1
OR

3. In the circuit below (figure 2), determine the current in 12V source and the voltage across 3A source using superposition theorem. [10]

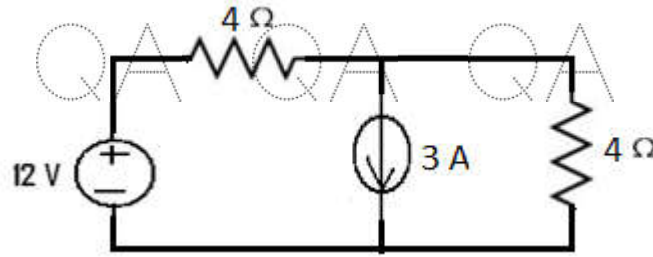


Figure 2

4. In the circuit below (figure 3), determine the value of k for the circuit to have resonance condition. Also determine the current, impedance of the circuit at resonance. Determine the half power frequencies, quality factor and bandwidth [10]

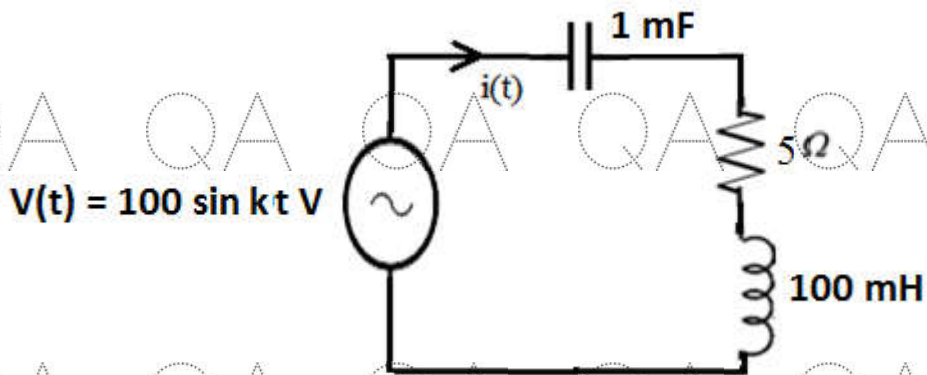


Figure 3

OR

5. Determine the power in all the circuit elements of the circuit below figure 4. [10]

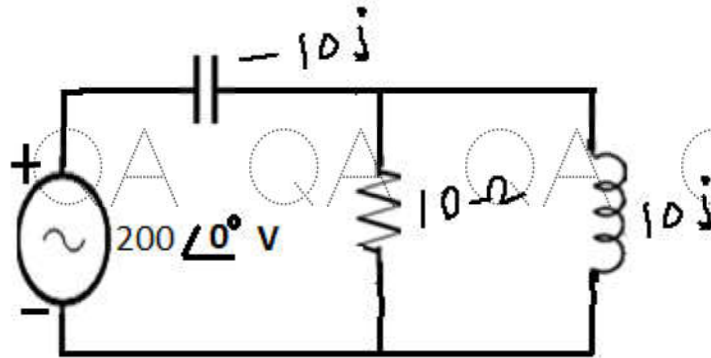


Figure 4

- 6.a) How the properties of practical transformer deviate from ideal transformer? Explain.
 b) Draw the circuit diagram of auto transformer. Explain the operational differences of it with two winding transformer. [5+5]

OR

QA QA QA QA QA QA QA QA

7.a) Explain the relationship between voltages in primary and secondary of delta-star three phase transformer connections.

b) Obtain the expression for the voltage regulation of single phase transformer for lagging load in terms of equivalent circuit parameters. [5+5]

8.a) Explain the constructional details of three phase induction motor.

b) Discuss about the working of synchronous generators. [5+5]

OR

9.a) Describe the working of separately excited DC motor.

b) What are the ways to start a 3-phase induction motor? Explain. [5+5]

10.a) Describe in detail about the working of ELCB.

b) What are the types of cables? Explain. [5+5]

OR

11.a) Describe in detail about the working of MCCB.

b) What is power factor? How to improve the low power factor? [5+5]

QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA