

R22

Code No: 183AP

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, December-2024/ January -2025

DIGITAL ELECTRONICS
(Common to CSE(IOT), AI&DS)

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.

i) **Part- A** for 10 marks, ii) **Part - B** for 50 marks.

- Part-A is a compulsory question which consists of ten sub-questions from all units carrying equal marks.
- Part-B consists of **ten questions** (numbered from 2 to 11) **carrying 10 marks each**. From each unit, there are two questions and the student should answer one of them. Hence, the student should answer five questions from Part-B.

PART- A

(10 Marks)

- Convert the following number to decimal (198)₁₂. [1]
- Give the 2's complement of 1000110110. [1]
- In Boolean logic, what does the term "minterm" refer to? [1]
- Which logic gate combination can replace an XOR gate in a digital circuit? [1]
- What is a multiplexer? [1]
- What is a priority encoder? [1]
- What is a ripple counter? How many flip-flops are required for a 3-bit ripple counter? [1]
- Define a "modulus counter." [1]
- What is the main purpose of a memory decoder in a RAM module? [1]
- What is the function of a Look-Up Table (LUT) in an FPGA? [1]

PART- B

(50 Marks)

- What is a Boolean function? Differentiate between canonical and standard forms of Boolean expressions with examples. Express the Boolean function $F(A, B, C) = A + BC$ in both SOP and POS form.
- Design a two-level implementation of the Boolean function $F = (A + B)(C + D)$ using NAND and NOR gates. [5+5]

OR

- Define Boolean Algebra and list its basic axioms. Also State and Prove DeMorgan's Theorem.
- Obtain the truth table of the following Boolean function, express the function in Sum of minterms and Product of Maxterms and also obtain the Dual and Complement of the function. $F = (xy + z).(y + xz)$. [5+5]

4.a) Explain the concept of "don't-care" conditions and their use in Boolean function minimization. Simplify the Boolean function $F(A, B, C, D) = \Sigma(0, 2, 5, 7, 8, 10, 12, 15)$ with don't-care conditions at $d(A, B, C, D) = \Sigma(1, 6, 11, 14)$ using a 4-variable K-map. Show the steps and final simplified expression.

b) Explain the properties of the Exclusive-OR (XOR) function and illustrate how it is used in arithmetic operations and error detection. Given the Boolean expression: $F(A, B, C) = A \oplus B \oplus C$ expand the function in terms of basic AND, OR, and NOT operations. [5+5]

OR

5.a) Explain two-level logic gate implementations. Using a two-level NAND-only implementation, simplify and implement the function $F(A, B, C, D) = AB + CD + \bar{A}\bar{C} + \bar{B}\bar{D}$. Draw the circuit and provide a detailed explanation of each simplification step.

b) Implement a logic circuit that represents a 5-input majority function, where the output is high if three or more inputs are high. Using K-map minimization, simplify the Boolean expression and implement it using only NAND gates. [5+5]

6.a) Design a 3-to-8 decoder circuit and explain how it can be used to implement any Boolean function of three variables.

b) Write a VHDL code to implement a 4-bit binary adder. Describe each part of the code, including entity, architecture, and signal declaration. [5+5]

OR

7.a) Design a 4-to-1 multiplexer circuit using basic logic gates. Show how this multiplexer can be used to implement any 2-variable Boolean function.

b) Design a 4-bit magnitude comparator circuit using basic logic gates. Explain how you can determine if one number is greater than, equal to, or less than another number using this circuit. [5+5]

8.a) A clocked sequential circuit has one input X and one output Z. The output Z is "1" if and only if the input X has been "1" for exactly two consecutive clock cycles. Derive the state diagram for this circuit, identify the states, and explain the transition conditions.

b) Design a 3-bit asynchronous (ripple) down-counter. Draw the circuit diagram and timing diagram to show its operation from an initial count of "111" to "000." [5+5]

OR

9.a) Design a sequence generator that outputs the sequence "001, 011, 101, 111" continuously. Show the state diagram, state table, and the resulting flip-flop excitation table. Identify the flip-flop type best suited for implementing this sequence generator and justify your choice.

b) Explain the operation of a Parallel-In Parallel-Out (PIPO) shift register. How can this type of register be used in data processing applications? Design a 4-bit PIPO shift register using D flip-flops. [5+5]

QA QA QA QA QA QA QA G

10.a) Implement the Boolean function $F = AB + \bar{A}C$ using a PAL. Show the configuration of the PAL and explain how each input is connected to generate the function.

QA QA QA QA QA QA QA G

b) Design a 2x4 ROM that stores the binary numbers "1001," "1100," "0110," and "0011" in each address. Show the circuit diagram and explain the operation of ROM for any one address input. [5+5]

OR

11.a) Define memory decoding. Design a memory decoder for a 4x8 memory system and explain how it helps in accessing specific memory locations within the system.

QA QA QA QA QA QA QA G

b) Design a 4x4 memory array with 4-bit words using SRAM cells. Draw the circuit diagram and explain the read and write operations in detail. [5+5]

QA QA QA QA QA QA QA G

---ooOoo---

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G