

R13

Code No: 113BR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, February - 2024

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART - A

(25 Marks)

- 1.a) State the Superposition theorem. [2]
- b) State and explain Kirchhoff's laws. [3]
- c) Define root mean square value of an alternating quantity. [2]
- d) A series circuit has $R=100$ ohm and $C=20 \mu F$. At what frequency will the current lead the voltage by 30° . Draw the corresponding phasor diagram. [3]
- e) Define copper loss in a transformer. [2]
- f) Distinguish between Ideal and a practical transformer. [3]
- g) State the applications of d.c motors. [2]
- h) List the constructional details of DC generators. [3]
- i) Mention the essential features of measuring instruments. [2]
- j) Write the classification of measuring instruments. [3]

PART - B

(50 Marks)

- 2.a) Discuss the classification of sources in detail.
- b) Three resistances of 25Ω , 50Ω and 100Ω are connected in parallel. If the total current drawn is 32 A, calculate the current drawn by each resistor. [5+5]

OR

- 3.a) State and explain Thevenin's theorem.
- b) Write short notes on star-delta transformation. If R_{ab} , R_{bc} and R_{ca} are connected in delta, obtain the expressions for equivalent star connection. [5+5]

- 4.a) Explain the terms with respect to Alternating Quantity:

- i) Average value
- ii) Form factor

- b) How do you generate alternating emf and explain the terms phase angle and Amplitude. [5+5]

OR

QA QA QA QA QA QA QA G

5. An a.c. circuit consists of a resistance of 5 ohms, an inductance of 0.1 H, and a capacitance of 100 μ F, all in series. Determine for this circuit:

- a) Total Impedance
- b) Reactance
- c) Admittance
- d) Susceptance, and
- e) Conductance.

The supply frequency is 60 Hz.

[10]

6.a) Explain the working of transformer with a neat diagram.

b) Derive the emf equation of a single phase Transformer.

[5+5]

OR

7.a) Explain the necessary tests that are conducted on transformer to find the efficiency and regulation.

b) The efficiency of 400 / 200 V, 200 KVA transformer is 98.5% at full load and at 0.8 lagging power factor. Calculate the values of core loss and full load copper loss. [5+5]

8.a) Explain the differences between self-excited and separately excited DC generators.

b) Explain the concept of rotating magnetic field in induction Motor.

[5+5]

OR

9.a) Explain in detail about the production of torque in DC motors.

b) A dc machine induces an emf of 240 V at 1500 rpm. Find the developed torque for an armature current of 25 A. [5+5]

10. Explain the working of Attraction type moving iron instrument with a neat sketch. [10]

OR

11. What are the advantages and limitations of Permanent Magnet Moving Coil (PMMC) instruments? Explain its working principle. [10]

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G