

R16

Code No: 133AQ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, February - 2024

ELECTRONIC CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART – A

(25 Marks)

- 1.a) What are difference amplifiers and write their use? [2]
- b) List the benefits of h-Parameters. [3]
- c) Compare negative feedback and positive feedback and their uses. [2]
- d) Discuss how does negative feedback reduce distortion in an amplifier. [3]
- e) What is cross-over distortion? [2]
- f) Why even harmonics are cancelled out in Push Pull Amplifiers? [3]
- g) What are the applications of clamping circuit? [2]
- h) Discuss about the double ended clipping. [3]
- i) What is an electronic switch? [2]
- j) Name the methods of triggering in multi vibrators? Distinguish between them. [3]

PART – B

(50 Marks)

- 2.a) Sketch the circuit of a CB amplifier. Derive the expression for the voltage gain at low Frequencies.
- b) Draw the circuit diagram of Emitter follower and derive the equation for Voltage and current gains. [5+5]

OR

- 3.a) Analyze the effect of coupling and Bypass capacitors on low-frequency response of JFET amplifier.
- b) What is mean by square wave testing? Elaborate. [5+5]

- 4.a) With relevant information explain how the negative feedback improves stability, reduce noise and Increase input impedance.
- b) With a neat sketch, explain the working of a Colpitt's oscillator. [5+5]

OR

- 5.a) Discuss the classification of amplifiers based on feedback and write the effect of Feedback on Amplifier characteristics.
- b) Design a Hartley oscillator circuit with specified frequency and component values.[5+5]

QA QA QA QA QA QA QA QA QA

- 6.a) Define thermal resistance. Explain the thermal electrical analogy related to a transistor with heat sink.
- b) Explain and analyze a transformer coupled class A power amplifier and also define the total harmonic distortion with three point method. [5+5]

OR

- 7.a) Discuss the operation of complementary symmetry class B power class – A Amplifier with a diagram.
- b) Mention the importance of the position of operating point on output signal swing in class A amplifier and prove that its conversion efficiency is 25%. [5+5]

- 8.a) With the help of a neat circuit diagram and waveforms explain the working of a transistor clipper.
- b) Explain the response of an RC high -pass filter to behave as a good differentiator. [5+5]

OR

9. Sketch the response of RC High pass circuit for pulse input and Ramp input and derive the output equations for the above inputs. [10]

- 10.a) Draw and explain the Monostable multivibrator circuit along with its waveforms.
- b) What is mean by Triggering? Discuss different Triggering methods. [5+5]

OR

11. Describe the switching times of BJT by considering the charge distribution across the base-region. Explain this for cut off, active and saturation regions. [10]

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA