

**R16**

**Code No: 131AK**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech I Year I Semester Examinations, January/February - 2024**

**BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

**(Common to EEE, ECE, CSE, EIE, IT)**

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART - A**


**(25 Marks)**

- 1.a) Differentiate dependent and independent sources. [2]
- b) Define R.M.S value and Average value of sinusoidal wave. [3]
- c) Define Q factor. [2]
- d) What is the magnitude of impedance and current during resonance frequency in R-L-C series circuit? [3]
- e) Draw the Volt Ampere characteristics of PN diode. [2]
- f) Differentiate static and dynamic resistance of PN junction diode. [3]
- g) Draw the symbols for i) PNP and ii) NPN transistors. [2]
- h) How BJT used as an amplifier? [3]
- i) What is the pinch-off voltage of JFET? [2]
- j) Explain the method of biasing JFET. [3]

**PART - B**

**(50 Marks)**

- 2.a) Three resistors 8 ohms, 6 ohms and 10 ohms are connected in series to a battery of terminal voltage 24 volts. Find the current in the circuit, Potential Difference across each resistor and power dissipated in each resistor?
- b) Determine the current  $I$  in the circuit shown below figure-1, All the resistances are in ohms? [5+5]

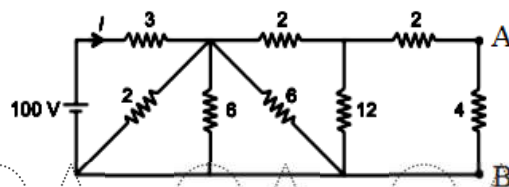

**Figure 1**  
**OR**

QA QA QA QA QA QA QA QA QA

3.a) Find the form factor for the below circuit.(Figure 2)

QA QA QA QA QA QA QA QA QA

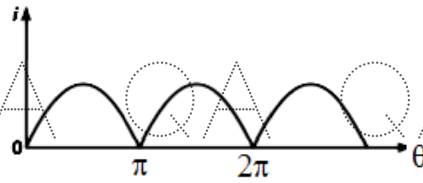


Figure 2

b) A pure inductance  $L = 0.2H$  has an applied voltage of  $e = 100 \sin 314t$ . Find the instantaneous and average power? [5+5]

QA QA QA QA QA QA QA QA QA

4.a) Calculate the current  $I_0$  using superposition theorem .(Figure 3)

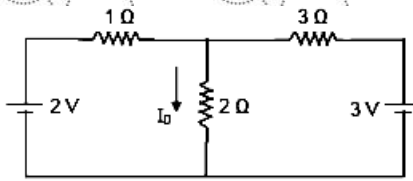


Figure 3

b) Draw the Thevenin's equivalent for the circuit shown in figure 4. [5+5]

QA QA QA QA QA QA QA QA QA

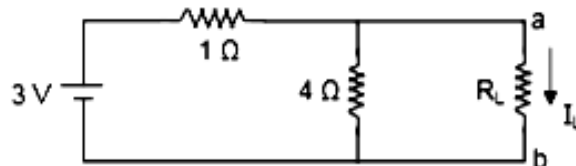


Figure 4

OR

5.a) Using Norton's theorem, determine current  $I_{ab}$  in the circuit shown in the figure 5.

QA QA QA QA QA QA QA QA QA

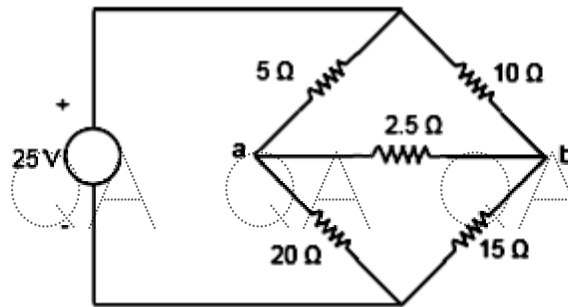


Figure 5

b) What should be the value of load resistor  $R$  in the circuit shown in figure 6 to dissipate maximum power? [5+5]

QA QA QA QA QA QA QA QA QA

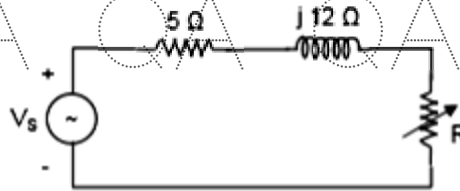


Figure 6

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA G

6.a) Explain the principle and operation of PN diode under forward and reverse biased conditions with necessary diagrams.

b) Write short notes on capacitor filter. [6+4]

QA QA QA QA QA QA QA G

7.a) Write short notes on inductor filter.

b) Explain the operation of half wave rectifier with necessary diagrams. [4+6]

8. Explain the working of Common Collector configuration of BJT with neat diagrams.

[10]

**OR**

9. Give detailed analysis of CE configuration of transistor using h-parameters.

[10]

QA QA QA QA QA QA QA G

10.a) Explain volt ampere characteristic of JFET.

b) Write the applications and advantages of JFET.

[5+5]

**OR**

11.a) Mention the difference between n-channel and p-channel JFET.

b) Compare BJT and FET.

[5+5]

QA QA QA QA QA QA QA G

--ooOoo--

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G