

Code No: 155SN

RA

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, July/August - 2023

LINEAR AND DIGITAL IC APPLICATIONS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART-A

(25 Marks)

- 1.a) Define CMMR and give its ideal and practical values. [2]
- b) Describe different configurations of differential amplifier. [3]
- c) Draw the pin diagram of IC 555 and explain each pin. [2]
- d) Why do we use higher order filters? Give the relationship between order of a filter and roll off rate? [3]
- e) Define the following terms with reference to DAC and ADC (Specifications):
i) Linearity ii) Monotonicity. [2]
- f) List out different A/D convertors and justify which A/D convertor is best in terms of speed. [3]
- g) Write the concept of CMOS transmission gate. [2]
- h) Write about magnitude comparator. [3]
- i) How to convert JK flip-flop to D flip flop? [2]
- j) Discuss how PROM, EPROM and EEPROM technologies differ from each other. [3]

PART-B

(50 Marks)

- 2.a) Draw the circuit of any one type of differential amplifier and explain the operation.
 - b) Describe the working of three terminal voltage regulator and mention its applications. [5+5]
- OR**
- 3.a) Explain the working of Inverting amplifier and derive the equation for its gain.
 - b) Derive the output voltage V_o of practical integrator circuit. [5+5]

- 4.a) Explain the operation of 2nd order band reject filter along with circuit diagram.
- b) Discuss about of the process of generating a square wave form with a neat circuit diagram. [5+5]

OR

- 5.a) Explain the operation of astable multivibrator using 555 timer and also derive the expression for frequency of oscillation.
- b) Draw the block diagram of 565 PLL and explain about each block. Make circuit connections to track the input signal and explain its operation. [5+5]

- 6.a) Explain the weighted resistor type DAC. Mention its applications.
b) With neat schematic, explain the operation of a counter type Analog to Digital converter. [5+5]

OR

- 7.a) Draw the circuit of weighted resistor DAC and derive expression for output analog voltage V_o .

- b) Explain the counter type ADC in detail. Mention its applications. [5+5]

- 8.a) Explain sinking current and sourcing current of TTL output? Which of the above parameters decide the fan out and how?

- b) Interpret Parallel binary adder with a circuit diagram. [5+5]

OR

- 9.a) Distinguish between static and dynamic power dissipation of a CMOS circuit. Derive the expression for dynamic power dissipation.

- b) Design a driving circuit for LED and which 74XX series IC is used for it. [5+5]

- 10.a) Design a 4-bit bidirectional shift register with parallel load.

- b) Design an 8×4 diode ROM using 74×138 for the following data starting from the first location. [5+5]

OR

- 11.a) Design a modulo 12 ripple counter using 74×74.

- b) With the help of timing waveforms, explain read and write operations of SRAM. [5+5]

---ooOoo---

QA QA QA QA QA QA QA (

QA QA QA QA QA QA QA (

QA QA QA QA QA QA QA (

QA QA QA QA QA QA QA (