

**R18**

**Code No:158CD**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B.Tech IV Year II Semester Examinations, July - 2023**

**POWER QUALITY AND FACTS  
(Electrical and Electronics Engineering)**

**Time: 3 Hours**

**Max. Marks: 75**

- Note:** i) Question paper consists of Part A, Part B.  
ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.  
iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART – A**

**(25 Marks)**

- 1.a) What are the causes of voltage swell? [2]
- b) List the remedies to improve power quality. [3]
- c) What is reactive-power control in electrical power transmission system? [2]
- d) What is the difference between active and passive reactive compensation? [3]
- e) What is a static VAR compensator? [2]
- f) Explain the basic operating principle of STATCOM. [3]
- g) What are the uses of FACTS devices? [2]
- h) Write the objectives of Series Compensators. [3]
- i) List the different functionalities of UPFC. [2]
- j) Draw the circuit diagram of Unified Power flow Controller. [3]

**PART – B**

**(50 Marks)**

2. Explain the terms Voltage sag, Voltage interruption, Voltage swells and Sag with harmonics with neat waveforms. [10]

**OR**

- 3.a) What is the impact of transients on power quality? Classify the transients that occur in power systems.

- b) What is harmonics? Explain harmonic distortion with relevant waveforms. [5+5]

4. Explain in detail about the Two – machine power system with an ideal midpoint reactive compensator with corresponding phasor diagram. [10]

**OR**

- 5.a) Explain why series compensation is more advantageous than shunt compensation?

- b) Explain the power oscillation damping in shunt compensation. [5+5]

6. Explain with a neat block diagram general control scheme of Static Var Compensator (SVC). [10]

**OR**

7. Explain basic Fixed Capacitor–Thyristor-Controlled reactor type Static Var Generator with a neat circuit and its output characteristics. [10]

QA QA QA QA QA QA QA G

8. Explain in detail, the basic operating principle and control scheme of TCSC. [10]

**OR**

QA 9. Explain in detail, the basic operating principle and control scheme of SSSC. [10] QA G

10. Explain the basic operating principles of UPFC with a conceptual representation. [10]

**OR**

11. Illustrate the conventional transmission control capabilities of the UPFC with the help of phasor diagrams. [10]

QA QA QA QA QA QA QA G  
---ooOoo---

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G