

**Note:** i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART - A**


**(25 Marks)**

- 1.a) What is the role of an instrument? [2]
- b) With an example, define KCL. [3]
- c) What is the purpose of armature winding in DC machines? [2]
- d) What is the function of Yoke? [3]
- e) What is a secondary winding? [2]
- f) Define synchronous speed. What is its importance? [3]
- g) Define reverse bias. [2]
- h) What is the relationship between input and output voltages of a half wave rectifier? [3]
- i) Define deflection. [2]
- j) What is the relationship between frequency and time period? [3]

**PART - B**

**(50 Marks)**

- 2.a) Describe in detail about star-delta transformations.
- b) For the circuit shown in the figure 1, find current 'I' and voltage 'V'. [5+5]

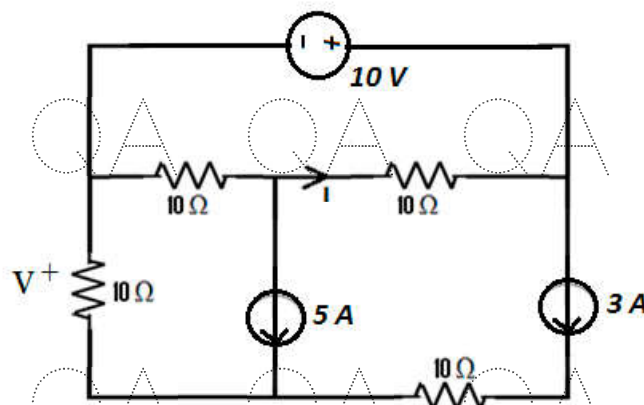

**Figure 1**  
**OR**

- 3.a) Describe the working of moving iron instrument in detail.  
 b) In the following circuit, find the voltages  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$ .(figure 2) [5+5]

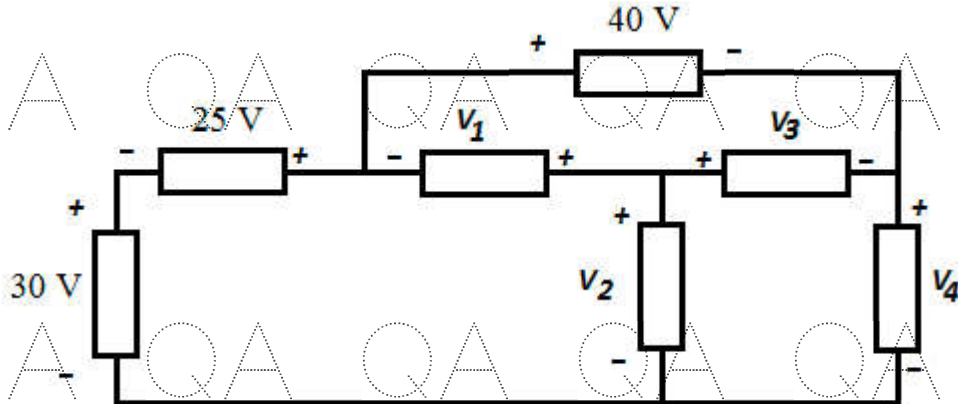


Figure 2

- 4.a) Explain the functions of stator and rotor in a DC machine in detail.  
 b) Describe briefly about different types of DC generators. [5+5]

OR

- 5.a) How EMF is induced in DC generator? Explain.  
 b) Derive the expression for torque in DC motor. [5+5]

- 6.a) What is an induction motor? How it works?  
 b) Across the HV side of a single phase 200V/400V, 50 Hz transformer, a resistance of  $10 \Omega$  is connected with LV side supplied with rated voltage and frequency. Determine the current and impedance seen by the supply. [5+5]

OR

- 7.a) Describe in detail about synchronous impedance method.  
 b) A 10 kVA, single phase transformer has a turns ratio of 5:1 and is supplied from a 2 kV supply. Neglecting Losses, determine (i) Primary current (ii) The full load secondary current (iii) The secondary Voltage [5+5]

- 8.a) Draw the V-I characteristics of PN junction diode and describe.  
 b) Draw the structure of PNP junction transistor and explain. [5+5]

OR

- 9.a) With the help of neat circuit and waveforms, explain the operation of full wave rectifier.  
 b) Draw the SCR characteristics and describe. [5+5]

- 10.a) What is the function of electron gun and glass envelope in CRT? Explain.  
 b) Describe briefly about the applications of CRO. [5+5]

OR

- 11.a) Describe in detail about electrostatic deflection.  
 b) How voltage is measured using CRO? Discuss. [5+5]