

Code No: 133BJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, September/October - 2023

NETWORK ANALYSIS

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART - A

(25 Marks)

- 1.a) Define self-inductance. [2]
- b) What is coefficient of coupling? [3]
- c) Define resonance in electrical circuits in detail, [2]
- d) Derive the current of the series RLC circuit subjected to sinusoidal voltage $v(t)$ considering the circuit as underdamped [3]
- e) What are the RMS and Average value of sinusoidal waveform? [2]
- f) Find the Laplace transform of i) unit step function ii) unit impulse function iii) unit exponential function. [3]
- g) Let the Laplace transform current $I(s)$ in a network is given by the following equation

$$I(s) = \frac{2}{(s+3)(s+5)}$$
 Plot the poles and zeros in the s plane. [2]
- h) A two-port network has the following z parameters $Z_{11} = 10$ ohms, $Z_{12} = Z_{21} = 5$ ohms, $Z_{22} = 12$ ohms. Compute the ABCD parameters for the same network [3]
- i) Give the design equations of symmetrical Π attenuator. [2]
- j) State and explain Foster's reactance theorem. [3]

PART - B

(50 Marks)

2. For the given resistance network (Figure 1) write a cut set matrix schedule and equilibrium equations on the voltage basis. Hence obtain the values of branch voltages and branch currents. Given that $R_1 = 5$ ohms, $R_2 = 5$ ohms, $R_3 = R_4 = R_6 = R_5 = 2$ ohms. [10]

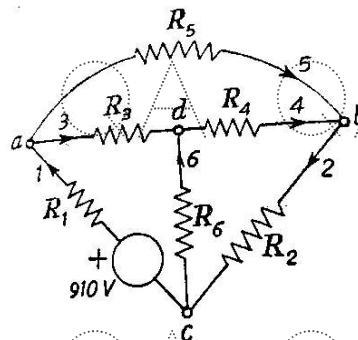


Figure 1

QA QA QA QA QA QA QA QA QA

OR

3. For the given resistive network (Figure 2) write a tie set schedule and obtain equilibrium equations on the current basis. Solve these equations and hence calculate the values of branch voltage and branch currents. [10]

QA QA QA QA QA QA QA QA QA

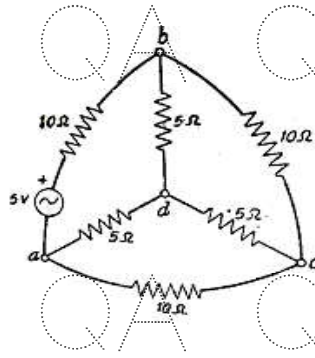


Figure 2

4. In the circuit shown in the following figure 3, the capacitor C_1 is initially charged to the voltage V_0 . At time $t=0$, the switch K is closed. Obtain the expressions for the (a) current and (b) charge across C_2 , as the function of time. If $C_1=C_2=1\mu\text{F}$, $V_0=10$ volts and $R=10$ ohms, calculate after the time $t = 10\mu\text{sec}$ (i) current (ii) voltage across R (iii) charge across C_1 and (iv) voltage across C_2 . [10]

QA QA QA QA QA QA QA QA QA

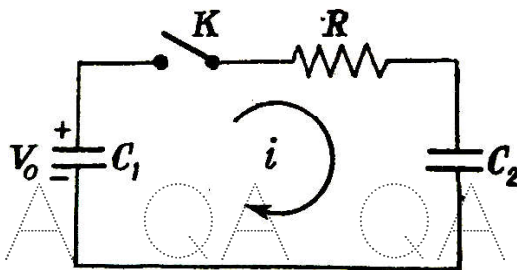


Figure 3

OR

5. In the given circuit in figure 4 the relay is adjusted to get operated at current of 7mili Amps. Switch K is closed at time $t=0$. It is found that the relay operates a $t=0.2$ sec. Find (a) inductance L of the relay coil and (b) Equation for the current $i(t)$. [10]

QA QA QA QA QA QA QA QA QA

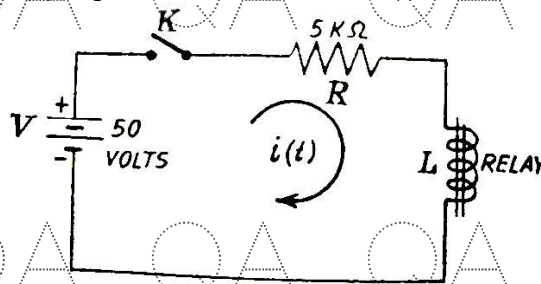


Figure 4

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA

6. A half cycle of the sine wave (Figure 5) of amplitude 10 volts periodic time 2π seconds, extending from $t=\pi$ seconds to 2π seconds is applied to the series RLC circuit consisting of the resistance $R= 12$ ohms and inductor $L= 2$ H and capacitor $C=0.1$ F. Find the current $i(t)$ [10]

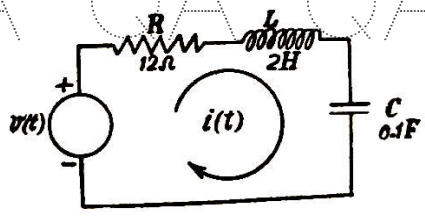
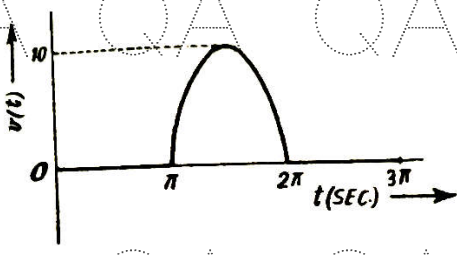


Figure 5
OR

7. A voltage pulse (Figure 6) of magnitude 8 volts and duration 2 seconds extending from $t = 2$ sec to $t = 4$ seconds is applied to the series R-L network consisting of $R=2$ ohms and $L= 1$ henry. Obtain the current $i(t)$. Also calculate the voltage across inductor L and resistor R . [10]

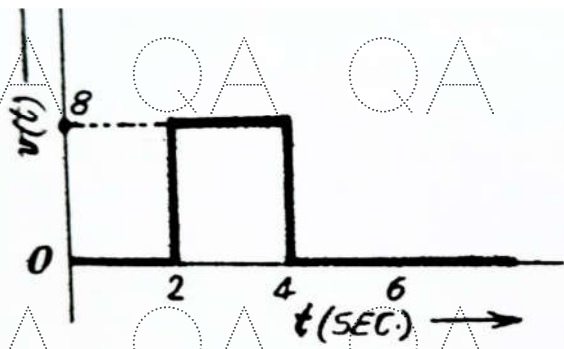


Figure 6

8. Find the Z parameters for the network shown in the Figure 7. [10]

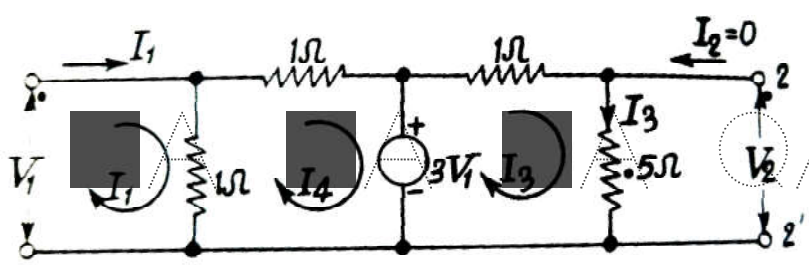


Figure 7
OR

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA

9. Derive the expression for ABCD parameters and Z parameters for the T section network shown in the figure 8 [10]

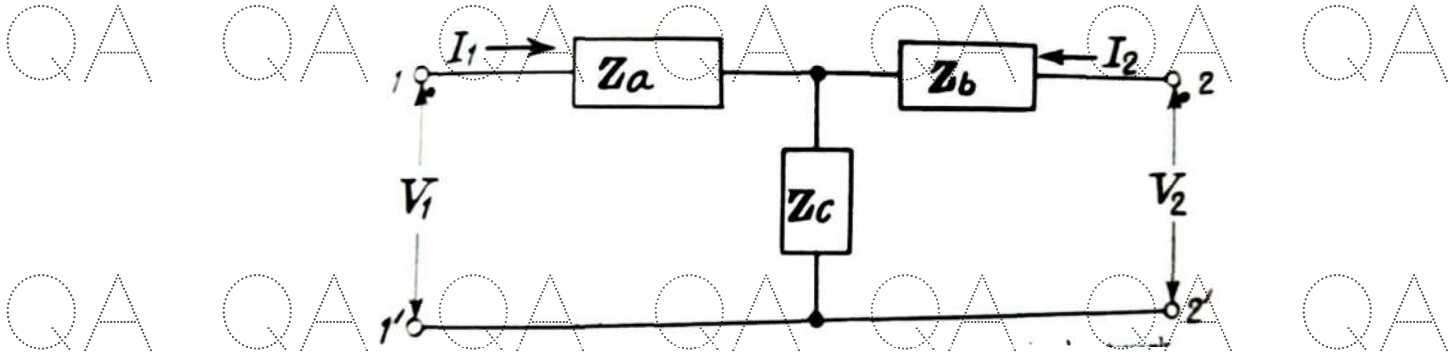


Figure 8

10. Discuss the design procedure of constant k-low pass filter. [10]

OR

11. Discuss the design procedure of constant k-high pass filter. [10]

QA QA QA QA QA QA QA QA QA

--ooOoo--

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA

QA QA QA QA QA QA QA QA QA