

**R18**

**Code No: 153AB**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech II Year I Semester Examinations, September/October - 2023**

**ANALOG AND DIGITAL ELECTRONICS**

**(Common to CSE, IT, ECM, ITE, CE(SE), CSE(CS), CSE(N))**

**Time: 3 Hours**

**Max. Marks: 75**

**Note:** i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART – A**

**(25 Marks)**

- 1.a) Define Ideal diode and practical diode. [2]
- b) Explain the basic principle operation of an LED. [3]
- c) What are the reasons for using multi-stage CE amplifiers? [2]
- d) What is thermal runaway in the context of transistors, and why is it a concern in amplifier design? [3]
- e) What does JFET stand for, and what type of transistor is it? [2]
- f) Compare various logic families in terms of their characteristics and applications. [3]
- g) List the applications of decoders. [2]
- h) Which are universal gates? Why they called so? [3]
- i) What is an excitation table? Draw the excitation table for SR Flip Flop. [2]
- j) Describe the concept of state reduction in sequential circuit design. [3]

**PART – B**

**(50 Marks)**

2. Define clipper and explain any '3' types of clippers. With the help of input and output wave forms and transfer characteristics. [10]
- OR**
3. Explain tunnel diode operation with the help of energy band diagrams. [10]
4. What is meant by bias compensation? Explain Diode Compensation Techniques. [10]
- OR**
5. Describe the operating principle of an emitter follower amplifier. How does it differ from a CE amplifier in terms of input and output characteristics? [10]
6. Describe the Common Source (CS) amplifier configuration. What are its key characteristics, and how does it provide voltage amplification? [10]
- OR**
7. Explain the operation of 3-input DTL NAND and NOR gates in detail. [10]

QA QA QA QA QA QA QA G

8. Design a 4-input priority encoder. [10]

**OR**

9. Find minimum sum of product form of the given function  $F(A,B,C,D) = \sum(1,3,5,6,7,12,14,15) + d(2,8,9)$  using K-Map and realize the circuit using NAND gates. [10]

QA QA QA QA QA QA QA G

10. Explain the operation of JK Flip flop and T-flip-flop with their characteristic tables. [10]

**OR**

11. Design a 4-bit asynchronous BCD counter using JK FF's. [10]

QA QA QA QA QA QA QA G

---ooOoo---

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G