

Code No: 153AN

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, September/October - 2023

DIGITAL SYSTEM DESIGN

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

- Note:** i) Question paper consists of Part A, Part B.  
 ii) Part A is compulsory, which carries 25 marks. In Part A, answer all questions.  
 iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

## PART-A

(25 Marks)

- 1.a) Given that  $(292)_{10} = (1204)_b$ , determine the value of b. [2]  
 b) Place the equation  $(A + \bar{B} + C)(\bar{A} + D)$  into proper minterm or maxterm canonical form. [3]  
 c) Describe the importance of don't care conditions. [2]  
 d) Implement half Adder using NAND Gates. [3]  
 e) State the need for preset and clear inputs of a flip-flop. [2]  
 f) Define asynchronous circuits. List any two drawbacks of asynchronous circuits. [3]  
 g) Differentiate fundamental mode and pulse mode asynchronous sequential circuits. [2]  
 h) What is ASM? Give the basic notations. [3]  
 i) Describe the specifications (i) Fan in and Fan out and (ii) Noise margin. [2]  
 j) Compare TTL, ECL and CMOS. [3]

## PART-B

(50 Marks)

- 2.a) How to detect and correct the error in the hamming code? Encode a binary word 11001 into the even parity hamming code.  
 b) Define and write about pros and cons of canonical form and differentiate with standard form. Express the Boolean function  $F = A + B'C$  as standard sum of minterms. [5+5]

OR

- 3.a) Find the standard sum of products (SOP) for the logic expression:  

$$F(A, B, C, D) = AB + \bar{A}B\bar{C} + B\bar{C}D$$
  
 b) Convert the following logic system into NOR gates only. As shown in figure 1. [5+5]

 


Figure 1

- 4.a) Using a 4 variable K map, simplify,  $F(A, B, C, D) = \sum m(1, 4, 9, 10, 11, 12, 14) + d(0, 8, 13)$   
 Realize the function using NAND gates only.  
 b) Implement the following Boolean functions with a multiplexer:  

$$F(w, x, y, z) = \sum(2, 3, 5, 6, 11, 14, 15).$$
 [5+5]

OR

- 5.a) Simplify the following switching functions using Quine McCluskey's tabulation method and realize expression using gates  $F(A, B, C, D) = \Sigma(0,5,7,8,9,10, 11, 14,15)$ .  
 b) Design a logic circuit that accepts a 4-bit gray code and converts it into 4-bit binary code. [5+5]

- 6.a) Discuss about static, dynamic and essential hazards in asynchronous sequential circuits.  
 b) Develop the logic circuit diagram and table for 4-bit ring counter and explain the working. [5+5]

**OR**

- 7.a) What is the drawback of JK flip-flop? How is it eliminated in Master Slave flip-flop? Explain with diagram.  
 b) Explain the difference between Ring and Johnson counters with neat sketch. [5+5]

- 8.a) Explain Mealy and Moore model of a clocked synchronous sequential network.  
 b) Design a clocked synchronous sequential logic circuit for the following state diagram. Use state reduction if possible, using D flip flops. As shown in figure 2. [4+6]

 


Figure 2

**OR**

- 9.a) Define state, present state, state diagram and state table.  
 b) Draw and explain the working of mod-18 counter using D-type flip-flop. [4+6]
- 10.a) Explain the working of open collector TTL NAND gate with circuit diagram.  
 b) Derive and discuss about CMOS dynamic electrical behaviour with characteristics. [5+5]

**OR**

- 11.a) What is meant by Tristate logic? Draw the circuit of Tristate TTL logic and explain the functions.  
 b) Explain about TTL to CMOS interfacing. [5+5]

--ooOoo--