

**R13**

Code No: 126AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, February - 2023

**STATIC DRIVES**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART - A**

**(25 Marks)**

- 1.a) What are the different modes of operation of 3- $\phi$  full converter fed DC drive? [2]
- b) Why semi converter is called half controlled rectifier? Draw its circuit diagram. [3]
- c) What is dual converter? [2]
- d) What is meant by dynamic braking? [3]
- e) What is four quadrant chopper fed DC drive? [2]
- f) What are the advantages and disadvantages of chopper fed d.c. drive. [3]
- g) What is Static Kramer's drive? [2]
- h) State the advantages and disadvantages of VSI and CSI drives. [3]
- i) What is self-control of synchronous motor? [2]
- j) Draw N-T(Speed-Torque) characteristics of synchronous motor with frequency control. [3]

**PART - B**

**(50 Marks)**

- 2.a) Starting from fundamentals, derive the speed torque relation for DC series motor.
  - b) Explain the principle of operation of 3- $\phi$  semi converter connected to DC series motor. [5+5]
3. Explain the neat sketches and the principle of operation of single phase fully controlled rectifier fed DC separately excited motor drive. [10]

**OR**

4. Explain four quadrant operation of DC separately excited motor fed from three phase dual converter. [10]
5. What is meant by braking? Explain Regenerative braking and Plugging applied to a d.c motor. [10]
6. Explain operation of two quadrant (Class D) chopper fed DC separately excited motor and also draw the current and voltage waveforms for continuous conduction. [10]

**OR**

7. Explain steady state analysis of Class A chopper fed DC separately excited motor. [10]

QA QA QA QA QA QA QA G

8.a) With the help of the block diagram, explain the closed loop operation of Induction motor drive?

QA QA QA QA QA QA QA G

b) Explain the speed control of induction motor by variable frequency control. [5+5]

**OR**

9. Explain the N-T(Speed-Torque) characteristics of induction motor with rotor resistance control. [10]

10. Explain the operation of CSI fed self-control of synchronous motor drive. [10]

**OR**

QA QA QA QA QA QA QA G

11. Explain the closed loop operation of synchronous motor drive with block diagram. [10]

**---ooOoo---**

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G