

**R18**

Code No: 156CJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, February - 2023

**POWER SEMICONDUCTOR DRIVES**

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Note: i) Question paper consists of Part A, Part B.

ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.

iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

**PART – A**

**(25 Marks)**

- 1.a) Draw the Speed – Torque Characteristics of DC series motor controlled by single phase semi converter. [2]
- b) What are the advantages and disadvantages of 3-phase fully controlled converters over single phase fully converters? [3]
- c) What do you mean by four quadrant operation? [2]
- d) Define Chopper and what are applications of Choppers? [3]
- e) How do you control the speed of an induction motor? [2]
- f) Draw the closed loop operation of induction motor with block diagram. [3]
- g) List out the applications of static Kramer's drive. [2]
- h) Explain the principle of slip power recovery used in control of induction motor. [3]
- i) What is PWM based Voltage Source Inverter? [2]
- j) Write the principle of self-control of synchronous motor. [3]

**PART – B**

**(50 Marks)**

2. Explain the operation of single phase semi-controlled converter connected to DC separately excited motor and obtain voltage current wave forms for continuous current operation. [10]

**OR**

3. Discuss the working of three phase fully-controlled converters connected to DC series motor and obtain voltage, current wave forms. [10]

4. Explain the operation of four quadrant chopper feeding to a DC separately excited motor and draw the wave forms for continuous current operation. [10]

**OR**

- 5.a) What is electric braking? Explain various types of braking.
- b) Explain the operation of two quadrant dc chopper fed separately excited dc motor. [5+5]

QA QA QA QA QA QA QA G

6.a) Explain the operation of variable frequency control of induction motor by Current Source Inverter.

b) Compare Voltage Source Inverter and Current Source Inverter. [6+4]

7. Explain the operation of variable frequency control of induction motor by cyclo converter with neat diagrams. [10]

OR

8. Explain the Static Scherbius drive operation of an induction motor with a circuit diagram. [10]

OR

9. Explain about static rotor resistance control of induction motor with neat diagram and draw the speed-torque characteristics. [10]

10. Explain the closed loop operation of synchronous motor drives with neat block diagram. [10]

OR

11. Describe VSI fed synchronous motor drive in detail with a suitable block diagram. [10]

QA QA QA QA QA QA QA G

---ooOoo---

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G

QA QA QA QA QA QA QA G